

# 數位系統設計實習

## Lecture 4

### CLA/Sequential Logic

指導老師: 陳勇志 教授

實習課助教: 黃柏皓

# Outline

2

- Verilog 複習 : Behavior-Level
- 4-bit Carry Look-ahead Adder
- Sequential Logic
- Latch and Flip-flop
- LAB 4-1 ~ 4-3

# Chapter

3

- Verilog 複習 : Behavior-Level
- 4-bit Carry Look-ahead Adder
- Sequential Logic
- Latch and Flip-flop
- LAB 4-1 ~ 4-3

# Recap Behavior Modeling

4

## □ Gate-level Modeling:

- 每個指令輸出只能1個位元

- \*信號必須是**wire**資料型態

- \*例如

- ```
xor g1(sum,A,B);
```

- ```
and g2(carry,A,B);
```

## □ Dataflow Modeling:

- 資料流敘述的前後次序不重要。

- \*出現在 = 敘述左邊的信號必須是**wire**資料型態

- \*例如 `assign out = A + B;`

## □ Behavior Modeling:

- **always**方塊內敘述的前後次序很重要。

- \*出現在 = 敘述左邊的信號必須宣告**reg**資料型態

- \*例如 `always@ (A,B) //always@(*)`

`out = A + B;`

- \*可以用行為來描述電路

- \*例如 if、elseif、case、for loop.....等

# Recap Behavior Modeling

## □ Initial Statement:

-從時間 0 開始

\*只執行一次

\*通常用於初始化、監控、波形

\*多個 **Initial block** 會並發執行

\*必須將多個行為語句分組，通常使用關鍵字 **begin** 和 **end**

## □ Always Statement :

-從時間 0 開始

\*以循環方式連續執行 **always** 區塊中的語句

\*用於對數位電路中連續重複的活動區塊進行建模

\*必須將多個行為語句分組，通常使用關鍵字 **begin** 和 **end**


# Recap Behavior Modeling

## Combinational

```
module combinational(a, b, sel,
                    out);

    input a, b;
    input sel;
    output out;
    reg out;

     always @ (a or b or sel)
    begin
        if (sel) out = a;
        else out = b;
    end
endmodule
```




## Sequential

```
module sequential(a, b, sel,
                 clk, out);

    input a, b;
    input sel, clk;
    output out;
    reg out;

     always @ (posedge clk)
    begin
        if (sel) out <= a;
        else out <= b;
    end
endmodule
```




# Chapter

7

- Verilog 複習 : Behavior-Level
- **4-bit Carry Look-ahead Adder**
- Sequential Logic
- Latch and Flip-flop
- LAB 4-1 ~ 4-3
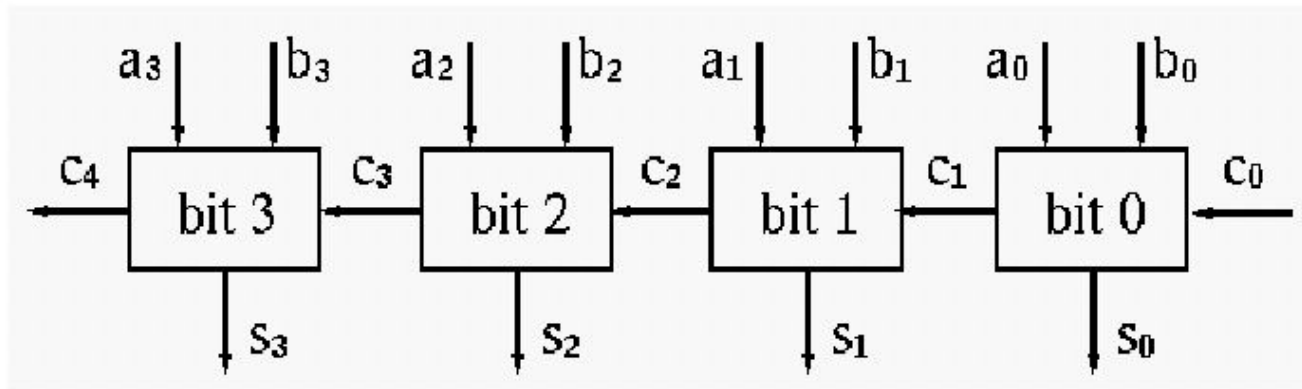
# 4-bit Carry Look-ahead Adder

- 傳統的 ripple carry adder 在做加法時須要等上一級的 carry out 產生後才能繼續下去，對於 16-bit adder，甚至於  $n$ -bits adder 所造成嚴重之 delay。




Ripple Carry Adder


- CLA 就是針對改善 delay 而設計出來的架構，其想法是希望將所有的進位一次運算完成。



# 4-bit CLA

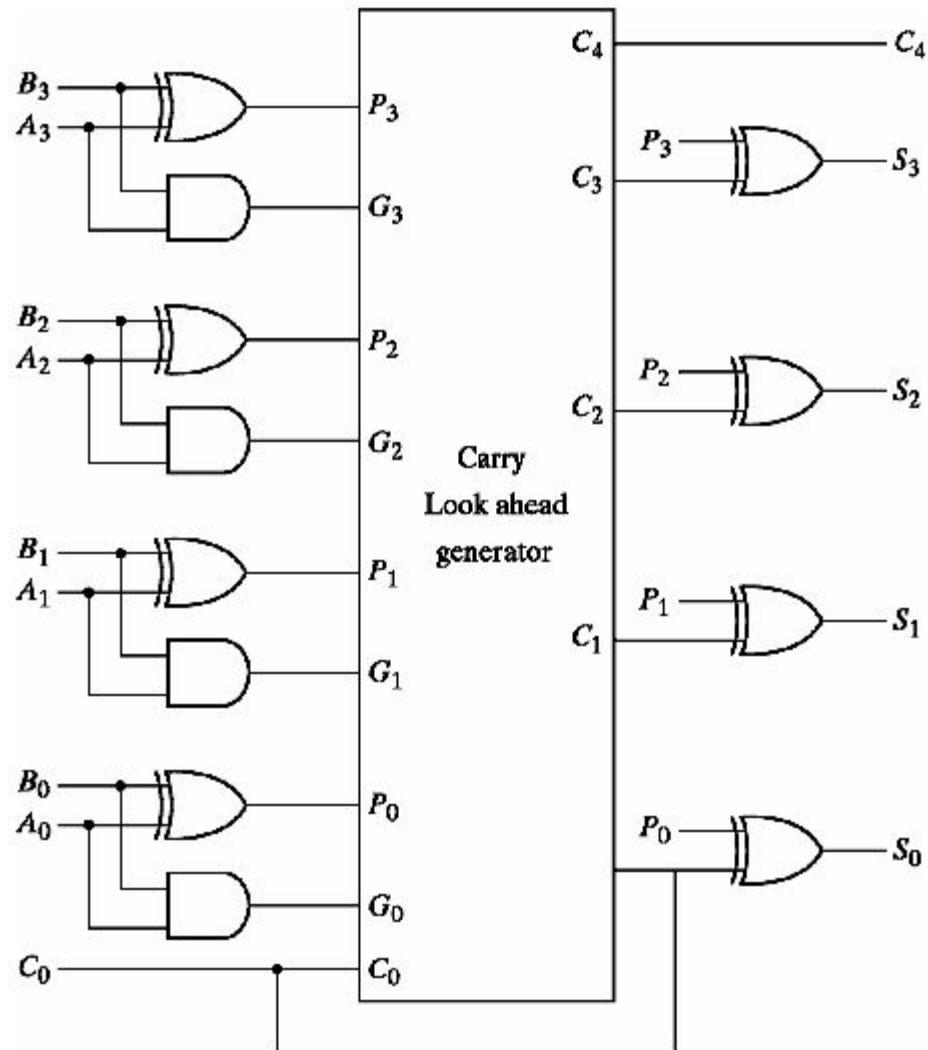

# 4-bit CLA

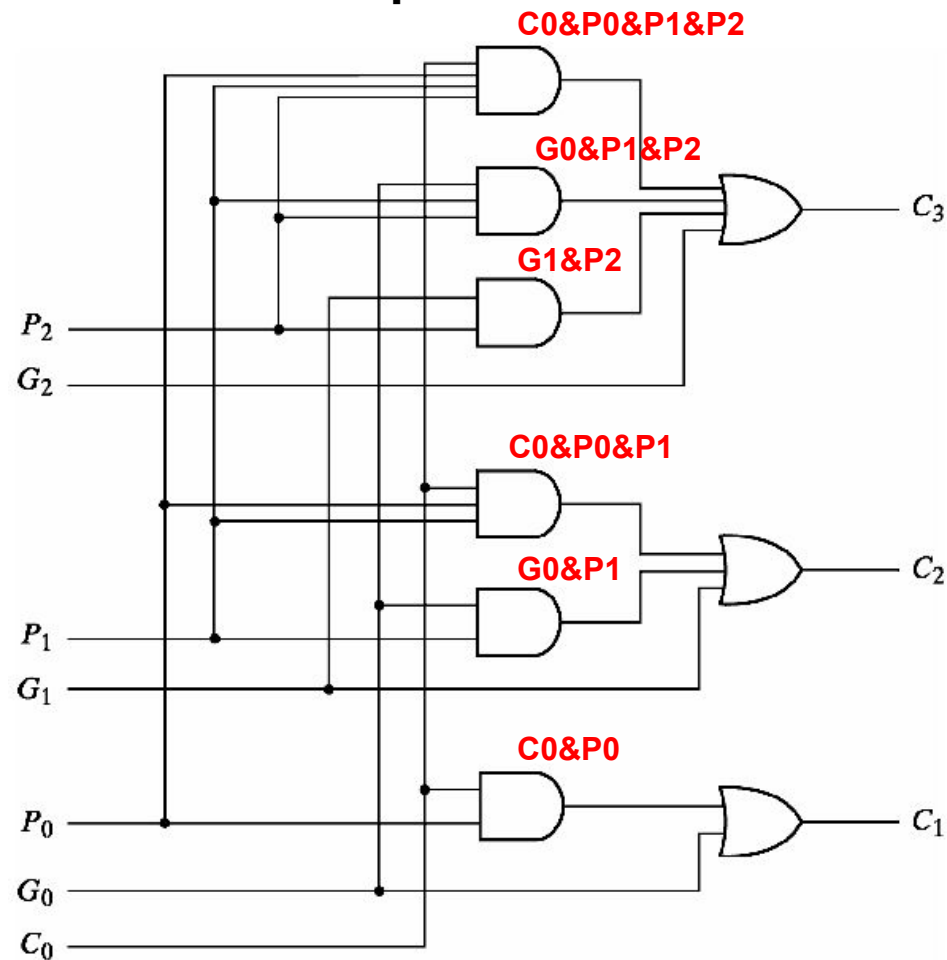

Carry Look-ahead Generator

# Chapter

11

- Verilog 複習 : Behavior-Level
- 4-bit Carry Look-ahead Adder
- **Sequential Logic**
- Latch and Flip-flop
- LAB 4-1 ~ 4-3


# Sequential Logic

## Combinational

```
module combinational(a, b, sel,
                    out);

    input a, b;
    input sel;
    output out;
    reg out;

     always @ (a or b or sel)
    begin
        if (sel) out = a;
        else out = b;
    end
endmodule
```




## Sequential

```
module sequential(a, b, sel,
                 clk, out);

    input a, b;
    input sel, clk;
    output out;
    reg out;

     always @ (posedge clk)
    begin
        if (sel) out <= a;
        else out <= b;
    end
endmodule
```



# Sequential Logic

## Blocking vs. Nonblocking:

Blocking ( = ), 具有**順序性**, 敘述會與先後有關係 ( 順序處理 )

Non-Blocking ( <= ), 具有**同時性**, 敘述與先後沒有關係 ( 平行處理 )


Blocking :

```
a = in;
```

```
b = a;
```

```
c = b;
```

```
//in=a=b=c
```

 


Nonblocking :

```
a <= in;
```

```
b <= a;
```

```
c <= b;
```

 

# Sequential Logic

## Blocking vs. Nonblocking:

```
input In;
reg [3:0] A, B, C;

always @( posedge CLK ) begin

    /* Blocking */           // 有順序執行，同C概念
    A[0] = In;               // 1CLK後A[0] = In
    A[1] = A[0];             // 1CLK後A[1] = A[0] = In
    A[2] = A[1];             // 1CLK後A[2] = A[1] = A[0] = In
    A[3] = A[2];             // 1CLK後A[3] = A[2] = A[1] = A[0] = In

    /* Non-Blocking */       // 同時執行，此範例有資料平移的效果
    B[0] <= In;               // 1CLK後B[0]存進In, B[1]存進B[0](存In之前的值)
    B[1] <= B[0];             // 2CLK後B[1]存進In
    B[2] <= B[1];             // 3CLK後B[2]存進In
    B[3] <= B[2];             // 4CLK後B[3]存進In
```

# Chapter

15

- Verilog 複習 : Behavior-Level
- 4-bit Carry Look-ahead Adder
- Sequential Logic
- **Latch and Flip-flop**
- LAB 4-1 ~ 4-3


# Latch and Flip-flop

- Latch 與 Flip-flop 均是數位電路中可以提供位元狀態儲存的裝置，它可以將邏輯狀態「0」或「1」存放在裝置內直到位元值需要改變或電源被切除。
- 由於有兩個穩定的輸出狀態，所以被稱為雙穩態電路。



# Latch and Flip-flop

- D latch :

 

(a) Logic diagram

$C$	$D$	Next state of $Q$
0	X	No change
1	0	$Q = 0$ ; Reset state
1	1	$Q = 1$ ; Set state

(b) Function table



# Latch and Flip-flop

- D latch :

```
module D_latch(D, control, Q);  
input D, control;  
output Q; //output reg Q;  
reg Q;  
always @(control or D)  
if (control) Q = D;  
endmodule
```

# Latch and Flip-flop

## □ Master-slave D Flip-flop :

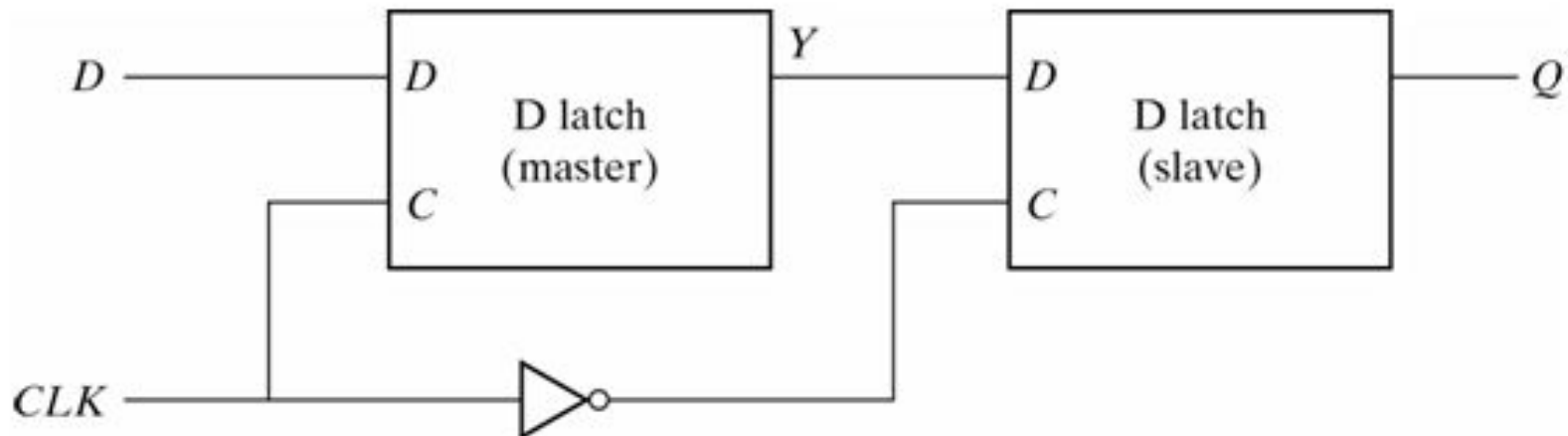 

# Latch and Flip-flop

- Characteristic Table of D Flip-flop :

$D_{\leftarrow}$	$Q(t+1)_{\leftarrow}$	
$0_{\leftarrow}$	0	(Reset) $_{\leftarrow}$
$1_{\leftarrow}$	1	(Set) $_{\leftarrow}$


# Latch and Flip-flop

- D Flip-flop:


```
module D_FF (D, CLK, Q);  
input D, CLK;  
output Q; //output reg Q;  
reg Q;  
always @(negedge CLK)  
    Q <= D; //Q = D;  
endmodule
```

# Latch and Flip-flop


## JK Flip-flop

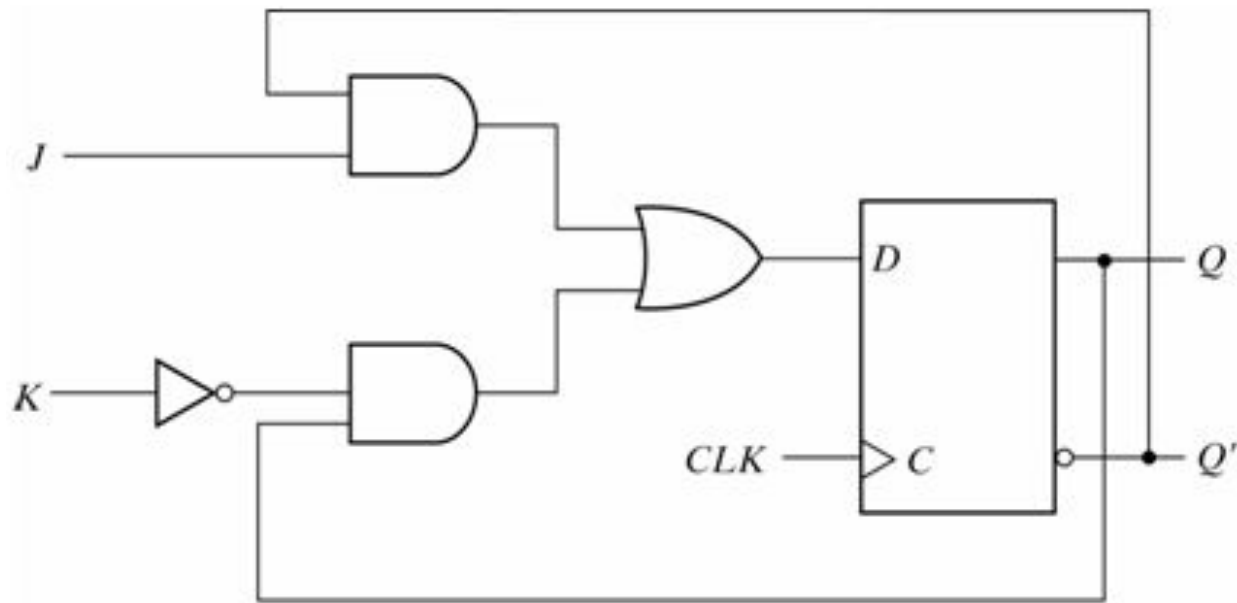

(a) Circuit diagram

 

(b) Graphic symbol

 

## JK Flip-flop 之時序圖

# Latch and Flip-flop


- Characteristic Table of JK Flip-flop :

$J_{\downarrow}$	$K_{\downarrow}$	$Q(t+1)_{\downarrow}$
0 <sub>↓</sub>	0 <sub>↓</sub>	$Q(t)$ (No change) <sub>↓</sub>
0 <sub>↓</sub>	1 <sub>↓</sub>	0 (Reset) <sub>↓</sub>
1 <sub>↓</sub>	0 <sub>↓</sub>	1 (Set) <sub>↓</sub>
1 <sub>↓</sub>	1 <sub>↓</sub>	$Q'(t)$ (Complement) <sub>↓</sub>




# Latch and Flip-flop


## □ T Flip-flop:

 

(a) From  $JK$  flip-flop

 


(b) From  $D$  flip-flop

 

(c) Graphic symbol

# Latch and Flip-flop

 

$T_{\phi}$	$Q(t+1)_{\phi}$
$0_{\phi}$	$Q(t)$ (No change) $_{\phi}$
$1_{\phi}$	$Q'(t)$ (Complement) $_{\phi}$

Characteristic Table of T Flip-flop

# Chapter

27

- Verilog 複習 : Behavior-Level
- 4-bit Carry Look-ahead Adder
- Sequential Logic
- Latch and Flip-flop
- **LAB 4-1 ~ 4-3**

# LAB 4-1


- 4-bit Carry Look-ahead Adder, A[3:0]、B[3:0]及C0為輸入，輸出為S[3:0]及C4，請使用Verilog HDL描寫出，並於Quartus II 模擬訊號波型加以驗證結果。

```
input [3:0]A,B;  
input C0;  
output [3:0]S;  
output C4;
```

# LAB 4-1

29

## □ 課堂檢查

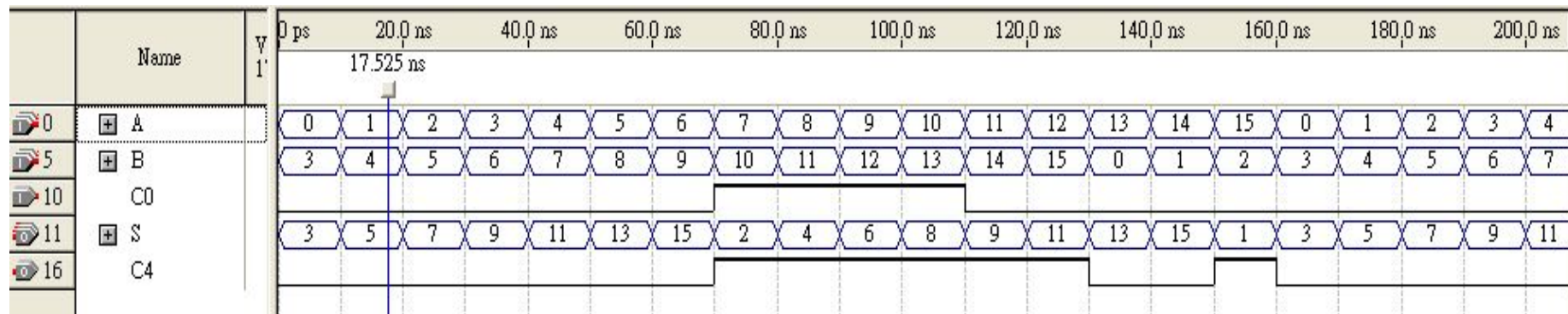


## LAB 4-2

- 請寫出含有set及reset之JK正反器(負緣觸發、以behavior方式描述, set與reset跟隨clk動作, set與reset都是等於1時動作)。

# JK正反器

31

## □ 課堂檢查

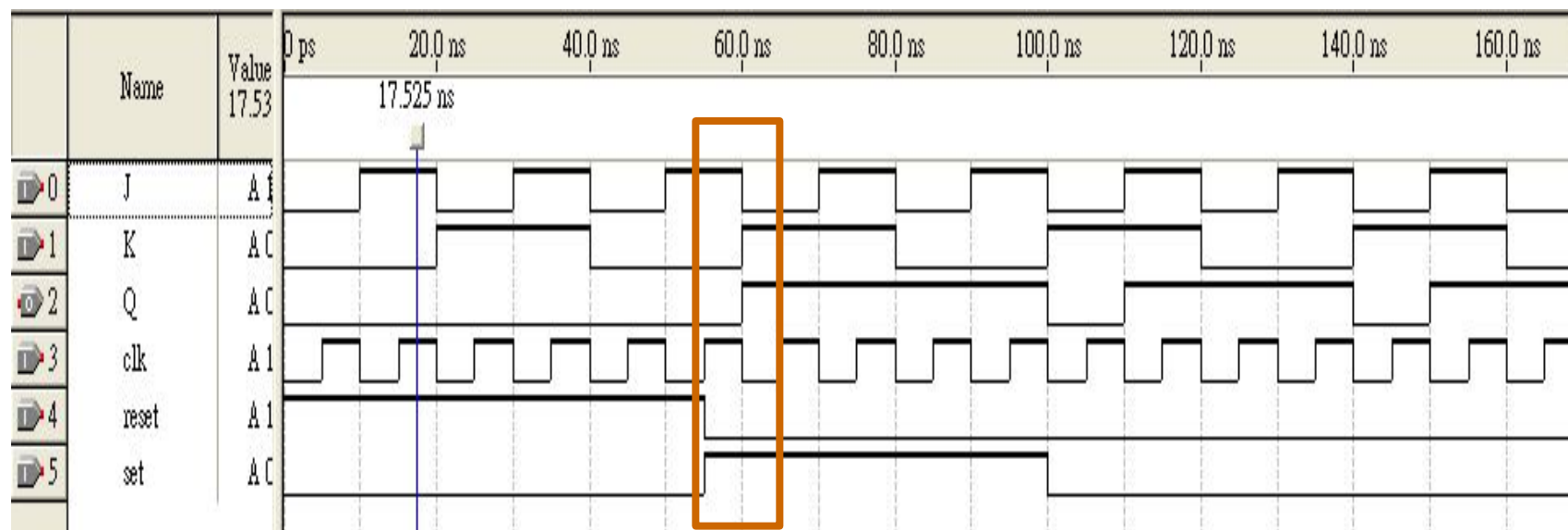

# LAB 4-3


- 使用Verilog HDL設計一個4位元具有平行輸入之暫存器，其輸入為D\_in[3:0], clk, rst, load,輸出為D\_out [3:0](clk為正緣觸發)。



# 4位元平行輸入之暫存器

33

## □ 課堂檢查

 

# LAB4

34

下課前將各Lab繳交至moodle：

上傳verilog.v

波形截圖